

Tables :-

OR gate :-

A	B	$A + B$
0	0	0
0	1	1
1	0	1
1	1	1

AND gate :-

A	B	$A \cdot B$
0	0	0
0	1	0
1	0	0
1	1	1

NOT gate :-

A	$y = \bar{A}$
0	1
1	0

NAND gate :-

A	B	$\overline{A \cdot B}$
0	0	1
0	1	1
1	0	1
1	1	0


Experiment - 1

Objective:- verification and interpretation of truth table for AND, OR, NOT, NAND, NOR Ex-OR, Ex-NOR Gates :-

Theory:- A logic gate is a kind of basic building block of a digital circuit having two inputs and one output. The basic logic gates are -


1. OR gate:- The OR gate output attains the state 1 when one or more inputs attain the state 1.

Boolean expression : $Y = A + B$

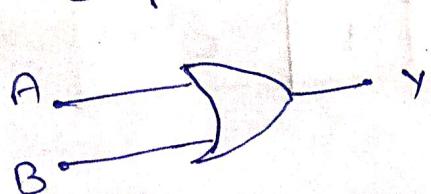

2. AND gate:- The AND gate outputs attains the state 1 only if both the inputs attain the state 1.

Boolean expression : $Y = A \cdot B$

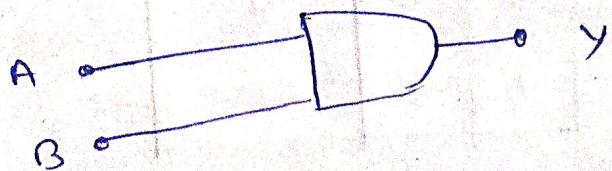

NOR gate :-

A	B	$A \oplus B$
0	0	1
0	1	0
1	0	0
1	1	0

XOR gate :-

A	B	$A \oplus B$
0	0	0
0	1	1
1	0	1
1	1	0

XNOR gate :-

A	B	$A \oplus B$
0	0	1
0	1	0
1	0	0
1	1	1

TUTORIAL / PRACTICAL NO.


3. NOT gate :- NOT gate inverts the input state.
if input is 1 output is 0 and vice versa
Boolean expression :- $y = \bar{A}$



4. NAND gate :- The digital circuit with the output of logical AND of all inputs inverted.


Boolean expression :-

$$y = \overline{A \cdot B}$$

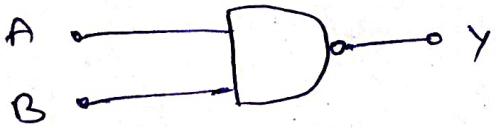

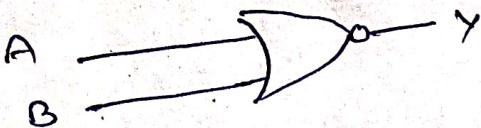
5. NOR gate :- Digital circuit with the output that is the logical OR of all those inputs inverted.

Boolean expression :- $y = \overline{A+B}$



6. XOR gate :- Digital circuit which outputs 0 if both inputs are same otherwise 1.

$$y = A \oplus B = A\bar{B} + \bar{A}B$$

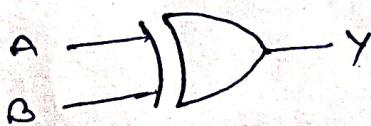


7. XNOR gate :- Digital circuit which outputs 1 only if the inputs are same.


$$y = \overline{A \oplus B} = \overline{A\bar{B} + \bar{A}B}$$



Circuit diagram:

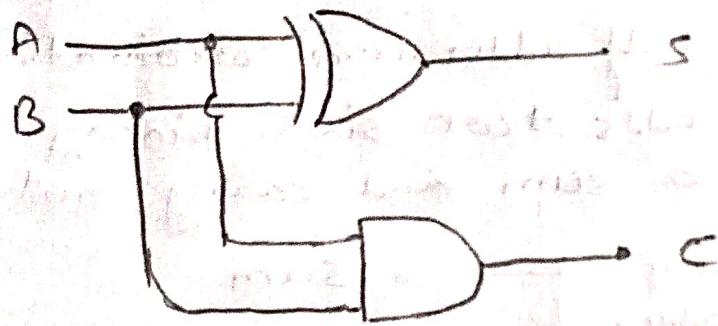

Half adder

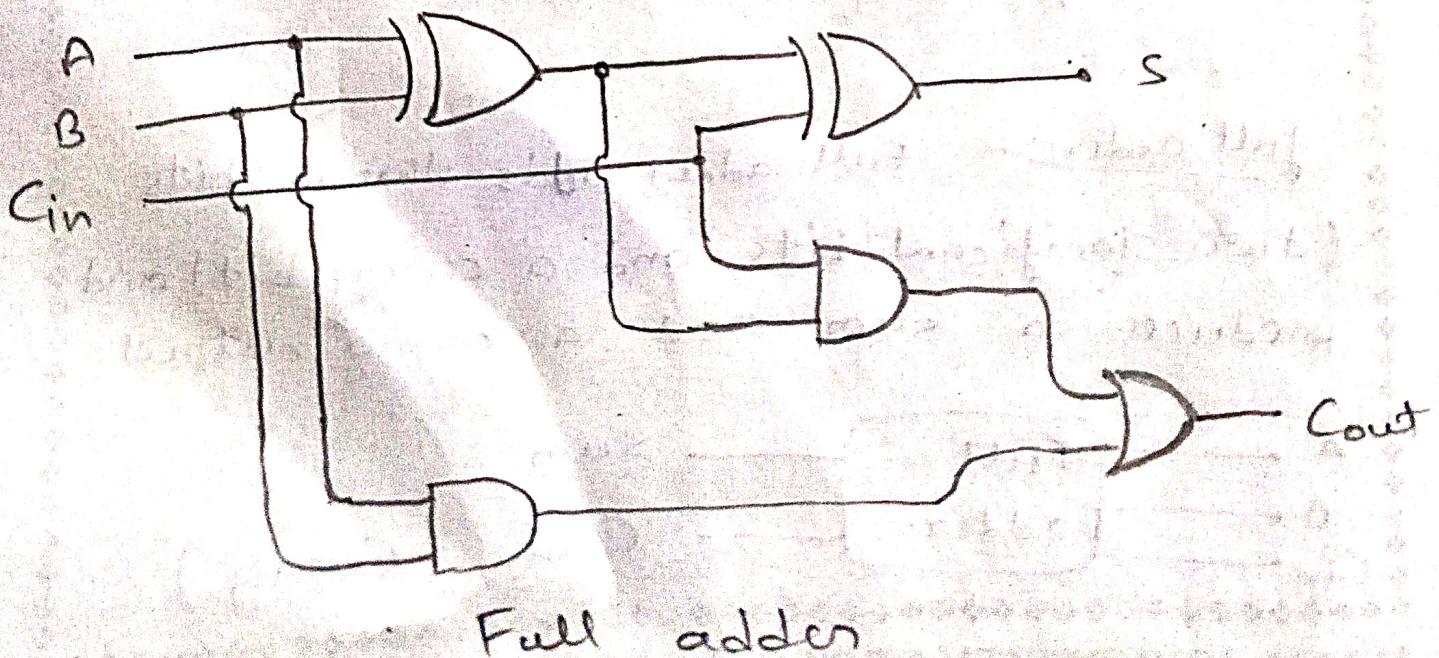


Full adder

Objective :- Construction of half and full adder using XOR and NAND gates and verification of it's application.

Theory:-

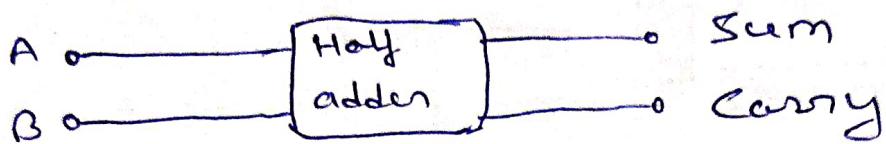Half adder Half adder is a combination circuit that adds two single binary digits and produce a sum and carry output.




$$\text{Sum} = A \oplus B \quad \text{Carry} = A \cdot B$$

Truth table:-

A	B	Sum(S)	Carry(C)
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

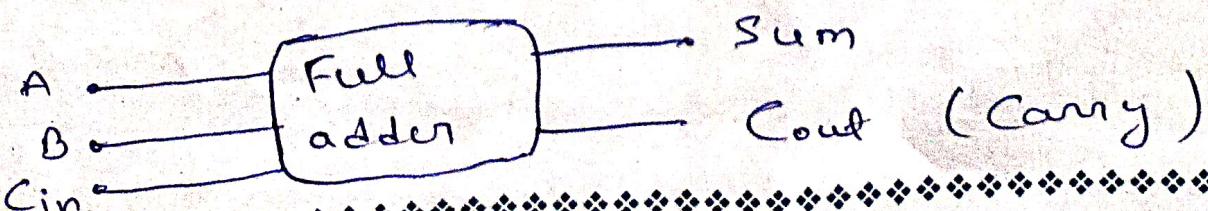full adder :- Full adder adds three bits (two significant bits and a carry bit) and produces a sum and a carry output.



Practical No.


$$\text{Sum} = A \oplus B \oplus \text{Cin}$$

$$\text{Cout (Carry)} = (A \cdot B) + (\text{Cin} \cdot (A \oplus B))$$


Truth-table:-

A	B	Cin	Sum	Carry
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

Circuit diagram :-

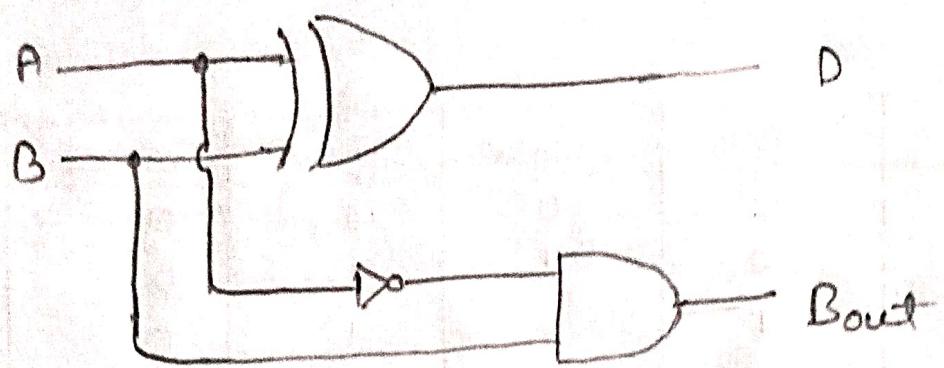

Half subtraction.

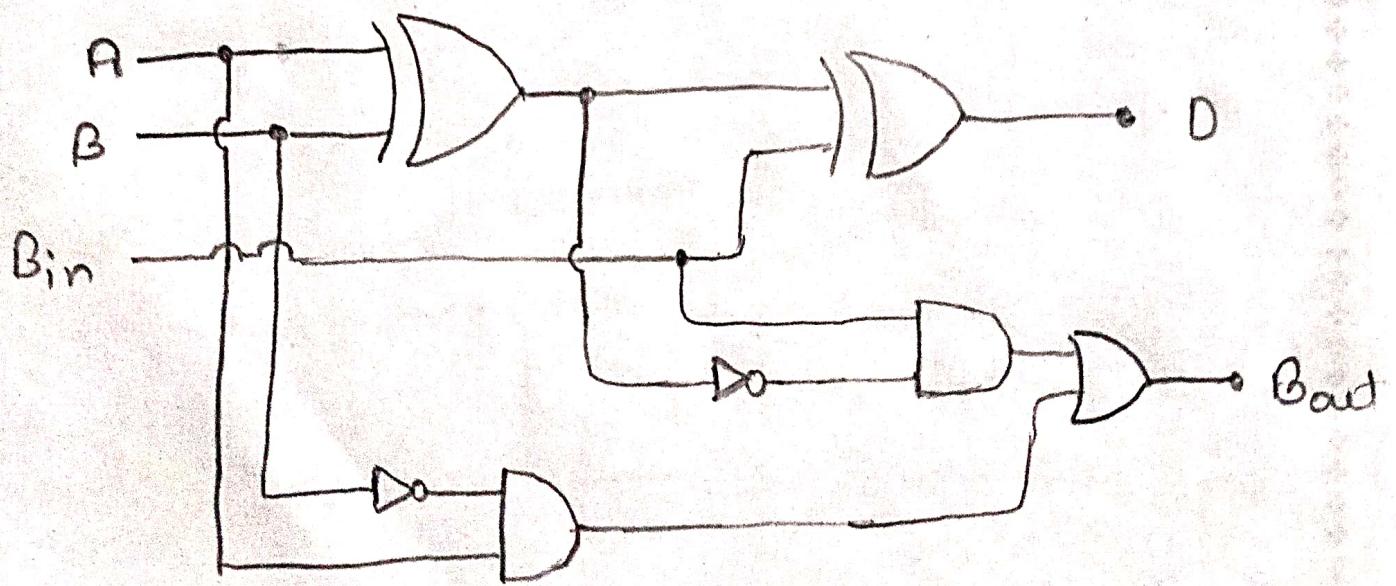

Full subtraction

Objective:- Study and verify half and full subtractor.

Theory:-

Half subtractor:- Half subtractor is a combinational circuit that subtracts two single binary digits and produces a difference and a borrow output.

$$\text{Difference} = A \oplus B$$

$$\text{Borrow} = \bar{A} \cdot B$$

Truth-table

A	B	Difference(D)	Borrow(B.ow)
0	0	0	0
0	1	1	1
1	0	1	0
1	1	0	0

Full subtractor:- A full subtractor subtracts three bits (two significant and a borrow bit) and produces a difference and a borrow output.

$$D = A \oplus B \oplus B_{in}$$

$$B_{out} = \bar{A} \cdot B + B_{in} \cdot (\bar{A} + B)$$

Truth-table :-

A	B	B_{in}	Difference(D)	Borrow
0	0	0	0	0
0	0	1	1	1
0	1	0	1	1
0	1	1	0	0
1	0	0	1	0
1	0	1	0	1
1	1	0	1	0
1	1	1	0	1