


UNIT-2

• Karnaugh Map (K-Map) -

2-variable K-Map -

$$f = \sum(0, 1, 3)$$


$$f = \bar{A} + B.$$

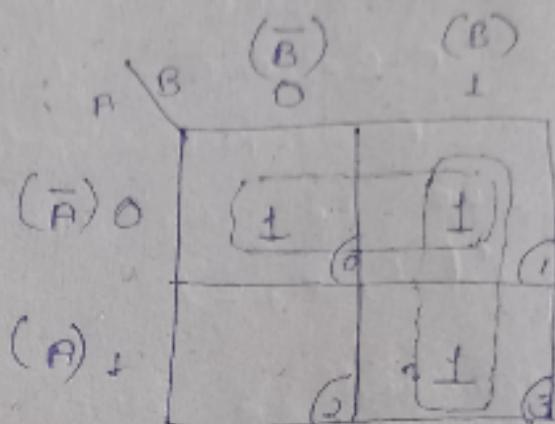

3-variable K-Map -

$$f = \sum(0, 1, 5)$$

$$= \bar{A}\bar{B} + \bar{B}C$$

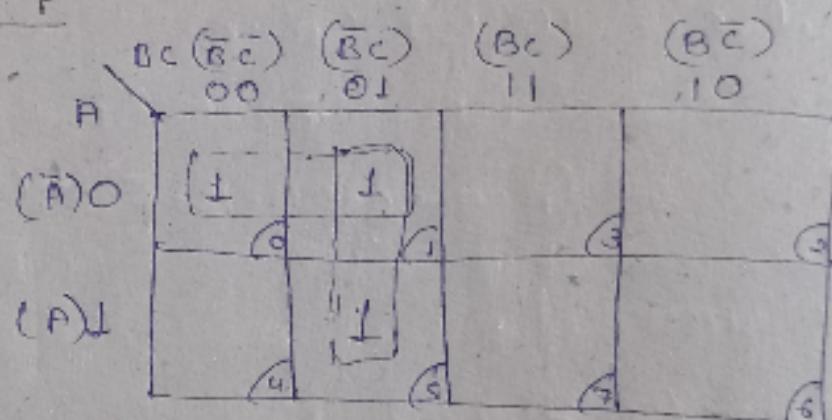


4-variable K-Map -

$$f = \sum(3, 4, 5, 7, 9, 13, 14, 15)$$

~~$= \bar{A}\bar{B}\bar{C}\bar{D} +$~~

$$A\bar{B}C + \bar{A}CD +$$

$$\bar{A}B\bar{C} + BD$$

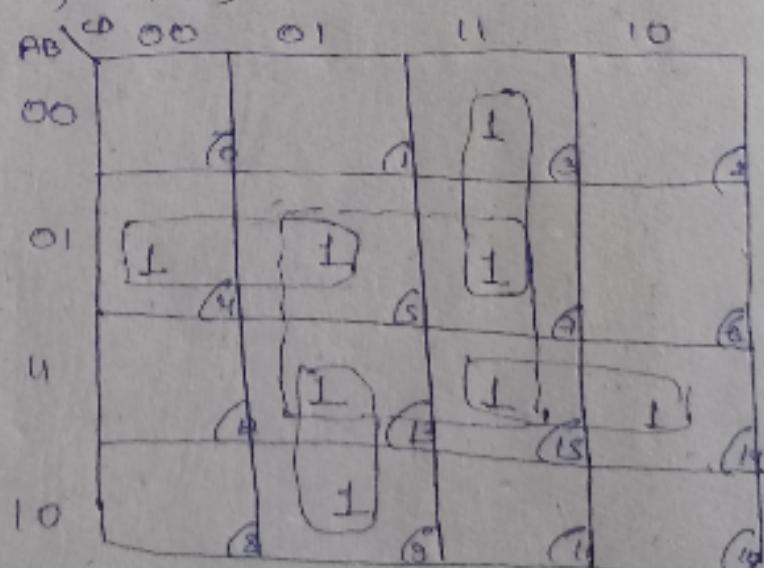

Don't care conditions -

Don't care combination -

Minimal expression in SOP form:

$$x \rightarrow 1$$

Minimal expression in POS form:

$$x \rightarrow 0$$

$$\text{Ex: } F_2(A, B, C, D) = \sum(5, 6, 9, 13, 15) + d(1, 7, 14)$$

Don't Cares

| AB | CD | 00 | 01 | 11 | 10 |
|----|----|----|----|----|----|
| 00 | 0 | 0 | X | 0 | 0 |
| 01 | 0 | 1 | 1 | 0 | 0 |
| 11 | * | 1 | 1 | 1 | X |
| 10 | 0 | 0 | 1 | 0 | 0 |

$$F_2(A, B, C, D) = BC + \bar{C}D$$

Don't care condition helps to minimise the no. of groups, hence, simplifying the expression.

The same above function can be written in POS form as

$$F_2(A, B, C, D) = \Sigma(0, 2, 3, 4, 8, 10, 11, 12) + d(1, 7, 14)$$

| AB | CD | 00 | 01 | 11 | 10 |
|----|----|----|----|----|----|
| 00 | 0 | 0 | X | 0 | 0 |
| 01 | 0 | 0 | 0 | X | 0 |
| 11 | 0 | 0 | 0 | 0 | X |
| 10 | 0 | 0 | 0 | 0 | 0 |

$$F_2' = \bar{B}C + \bar{C}\bar{D}$$

By De-Morgan's law

$$F_2' = (B + \bar{C}) \cdot (\bar{C} + \bar{D})$$


It is not important to include all the don't cares while forming equation but can be used if required.

Half Adder -


| A | B | Sum | Carry |
|---|---|-----|-------|
| 0 | 0 | 0 | 0 |
| 0 | 1 | 1 | 0 |
| 1 | 0 | 1 | 0 |
| 1 | 1 | 0 | 1 |

$$S = \overline{A}B + A\overline{B} = A \oplus B$$


$$C = AB$$

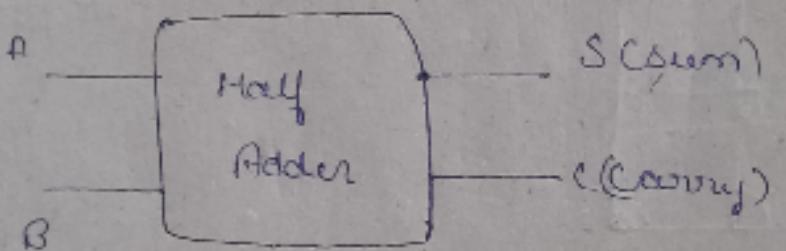

Logic Circuit -

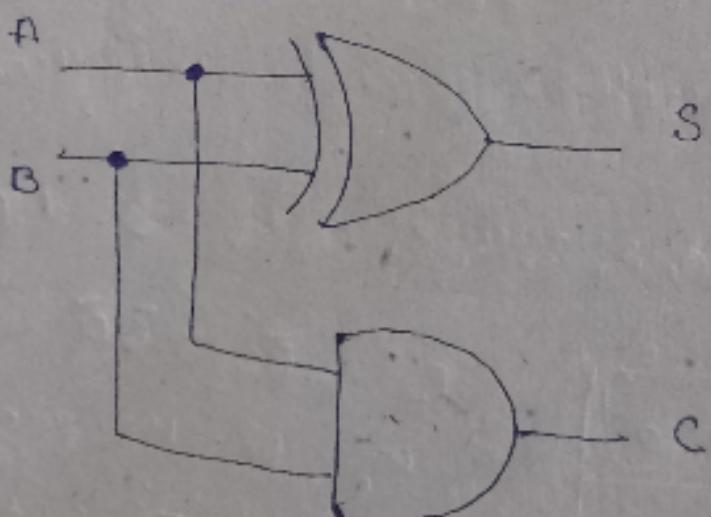

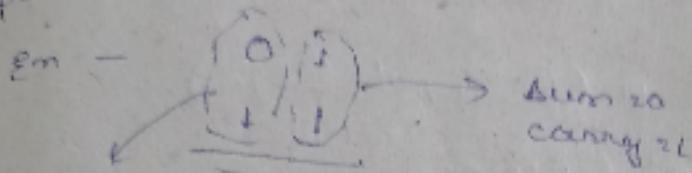Using the half adder we cannot generate the result if there is a carry from the previous operation.




This cannot be calculated using half adder because there is a carry 1.

For this we use Full adder.

Full Adder-

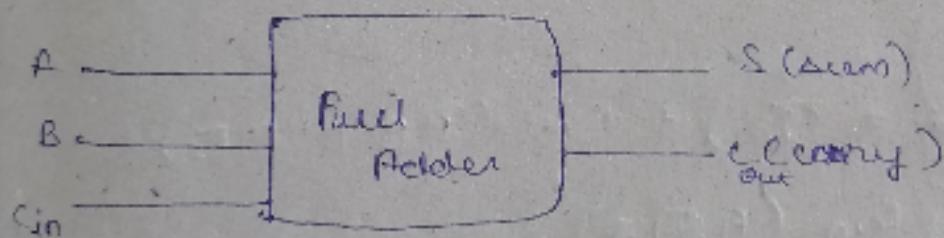Is used if you want to add a bit alongwith the carry bit.




| A | B | Cin | Sum | Cout |
|---|---|-----|-----|------|
| 0 | 0 | 0 | 0 | 0 |
| 0 | 0 | 1 | 1 | 0 |
| 0 | 1 | 0 | 1 | 0 |
| 0 | 1 | 1 | 0 | 1 |
| 1 | 0 | 0 | 1 | 0 |
| 1 | 0 | 1 | 0 | 1 |
| 1 | 1 | 0 | 0 | 1 |
| 1 | 1 | 1 | 1 | 1 |

Boolean expression of sum and carry -

$$\begin{aligned}
 S &= \overline{A}\overline{B}C_{in} + \overline{A}B\overline{C}_{in} + A\overline{B}\overline{C}_{in} + AB\overline{C}_{in} \\
 &= \overline{A}(\overline{B}C_{in} + B\overline{C}_{in}) + A(\overline{B}\overline{C}_{in} + B\overline{C}_{in}) \\
 &= \overline{B}(\underbrace{B \oplus C_{in}}_x) + A(\underbrace{\overline{B} \oplus \overline{C}_{in}}_{\bar{x}})
 \end{aligned}$$

$$G_{\text{out}}^z = \bar{A}Bc_{10} + A\bar{B}c_{10} + AB\bar{c}_{10} + A\bar{B}\bar{c}_{10}$$

Using Re-map -

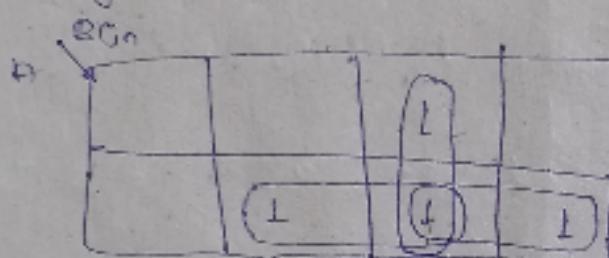


$$C_{\text{out}} = AB + BC\bar{a} + \bar{A}\bar{B}$$

四


$$\begin{aligned} C_{out} &= AB (\bar{C}_{in} + \bar{C}_{in}) + \bar{C}_{in} (\bar{A}B + A\bar{B}) \\ &= AB + \bar{C}_{in} (A \oplus B) \end{aligned}$$

$$C_{out} = AB + BC_{in} + AC_{in} = AB + C_{in}(A+B)$$


logic circuit -

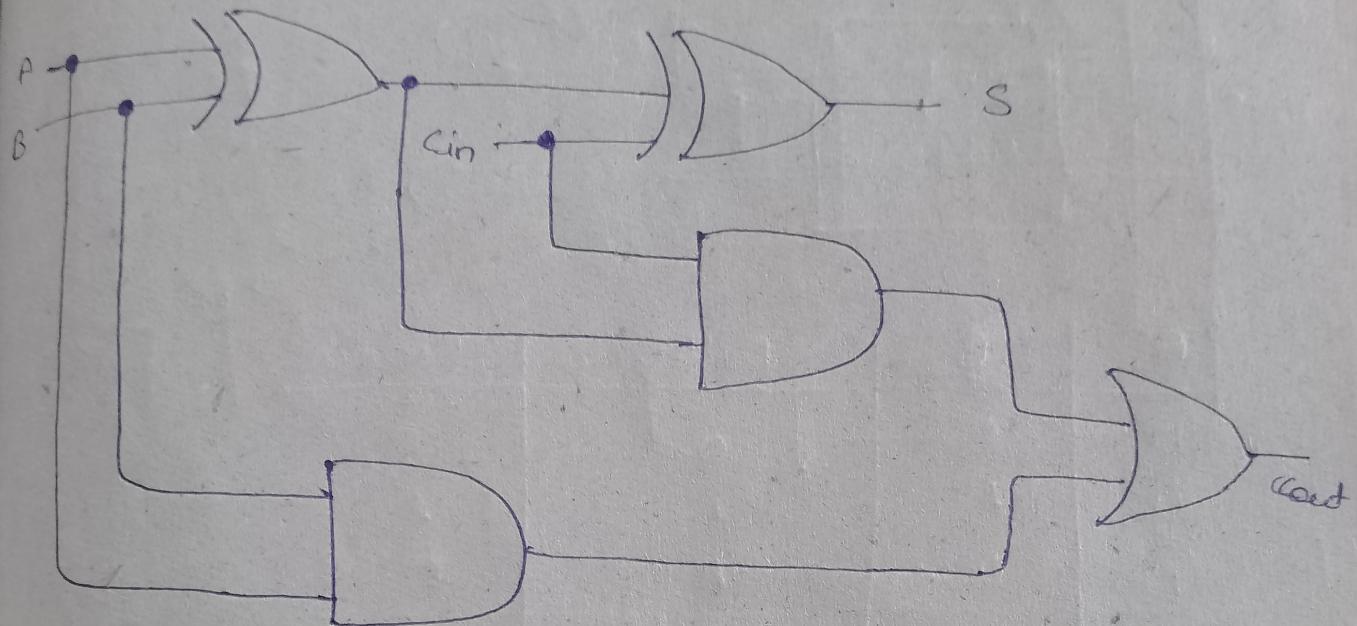

Full adder using half adders -

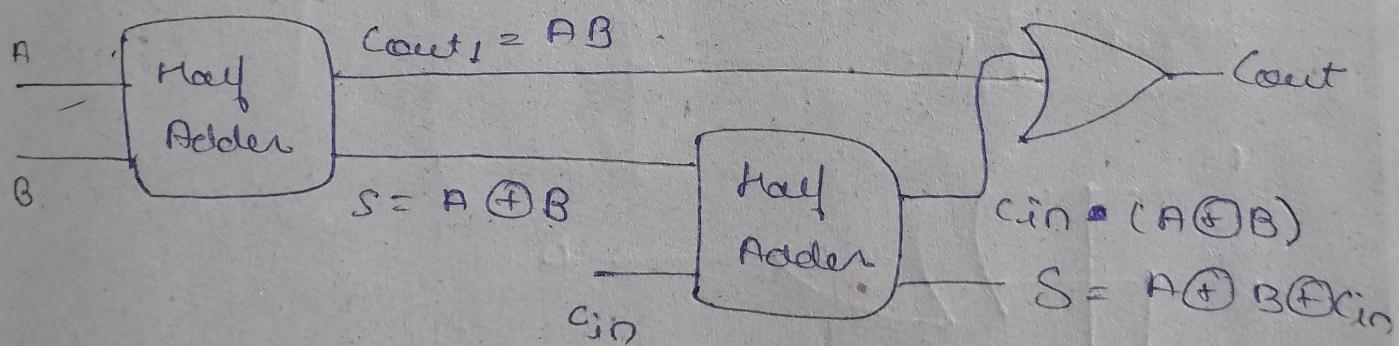


Half Subtractor -

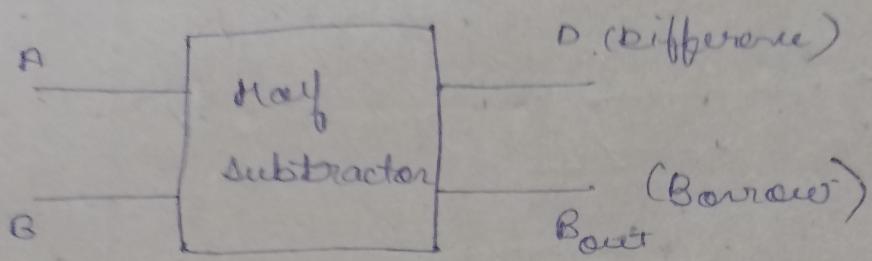


| A | B | Difference | Borrow |
|---|---|------------|--------|
| 0 | 0 | 0 | 0 |
| 0 | 1 | 1 | 1 |
| 1 | 0 | 1 | 0 |
| 1 | 1 | 0 | 0 |

$$D = \overline{A}B + A\overline{B} = A \oplus B.$$

$$B_{out} = \overline{A}B.$$

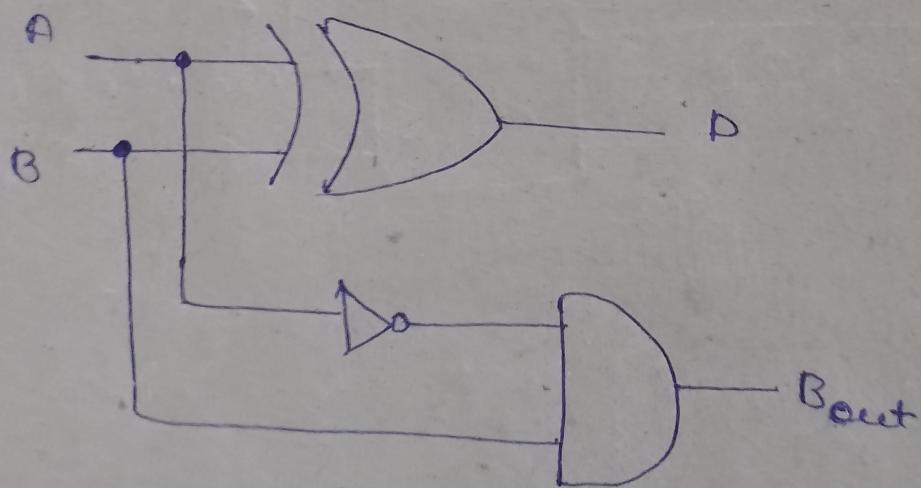

Full subtractor

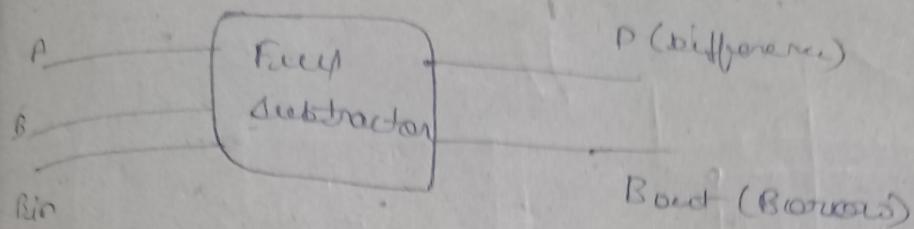

| A | B | Bin | D | B _{out} |
|---|---|-----|---|------------------|
| 0 | 0 | 0 | 0 | 0 |
| 0 | 0 | 1 | 1 | 1 |
| 0 | 1 | 0 | 1 | 1 |
| 0 | 1 | 1 | 0 | 1 |
| 1 | 0 | 0 | 1 | 0 |
| 1 | 0 | 1 | 0 | 0 |
| 1 | 1 | 0 | 0 | 0 |
| 1 | 1 | 1 | 1 | 1 |

$$D = \overline{A} \overline{B} \text{ Bin}_0 + \overline{A} B \overline{\text{Bin}}_0 + A \overline{B} \overline{\text{Bin}}_0 + A B \text{ Bin}_0$$

$$= \overline{A} (\overline{B} \text{ Bin}_0 + B \overline{\text{Bin}}_0) + A (\overline{B} \overline{\text{Bin}}_0 + B \text{ Bin}_0)$$

$$= \overline{A} (\underbrace{B \oplus \text{Bin}_0}_{\alpha}) + A (\underbrace{\overline{B} \oplus \overline{\text{Bin}}_0}_{\beta})$$


$$D = A \oplus B \oplus \text{Bin}_0$$

$$B_{out} = \overline{A} \overline{B} \text{ Bin}_0 + \overline{A} B \overline{\text{Bin}}_0 + \overline{A} B \text{ Bin}_0 + A B \overline{\text{Bin}}_0$$


$$= \overline{A} B (\text{Bin}_0 + \overline{\text{Bin}}_0) + \text{Bin}_0 (A B + \overline{A} B)$$

$$= \overline{A} \overline{B} + \text{Bin}_0 (A \oplus B)$$

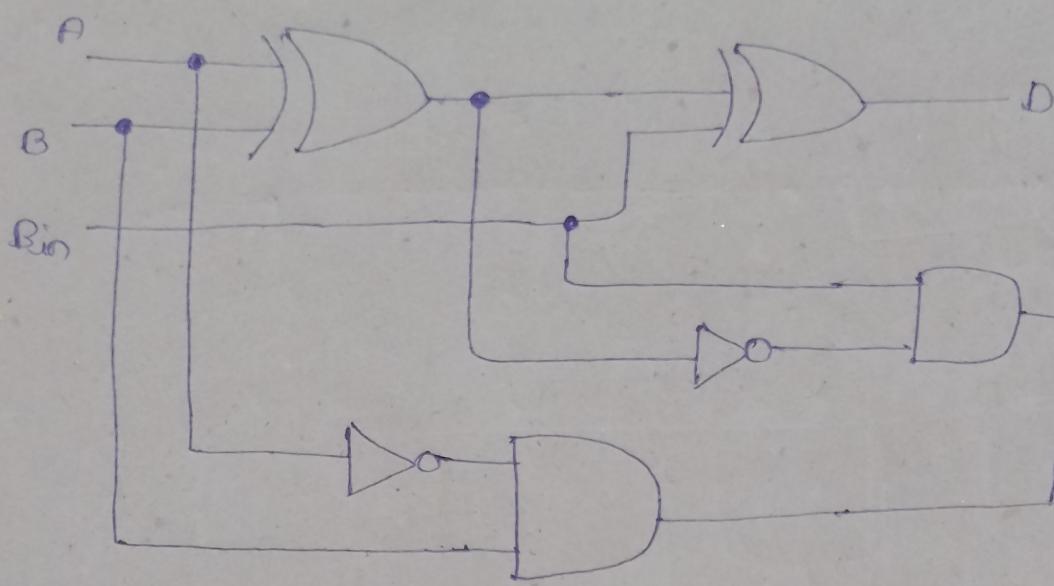
$$\boxed{B_{out} = \overline{A} B + \text{Bin}_0 (\overline{A} \oplus B)}$$



full subtractor using half subtractor -

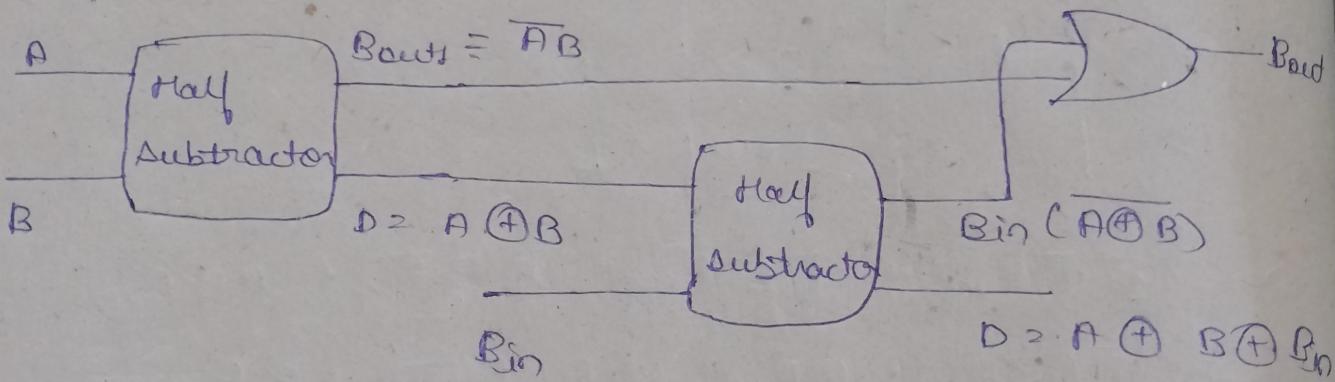

4-BIT ADDER AND SUBTRACTOR CIRCUITS

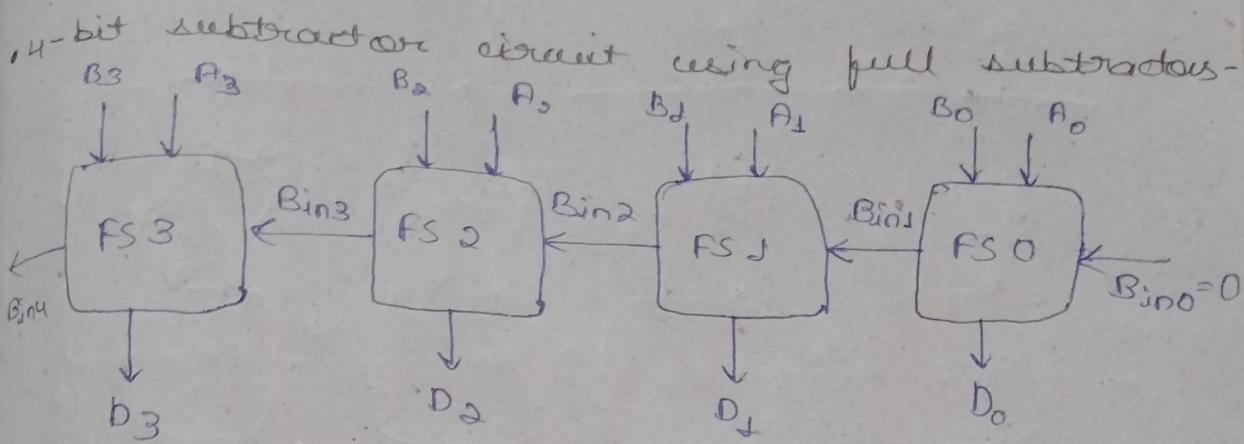

$$\begin{array}{r}
 A_3 \quad B_2 \quad A_1 \quad A_0 \\
 - B_3 \quad B_2 \quad B_1 \quad B_0 \\
 \hline
 D_3 \quad D_2 \quad D_1 \quad D_0
 \end{array}$$

$$\begin{array}{r}
 1 \quad 1 \quad 1 \quad 0 \\
 - 0 \quad 1 \quad 0 \quad 1 \\
 \hline
 0 \quad 1 \quad 0 \quad 0 \quad 1
 \end{array}$$


4-bit subtractor using adder circuit -

$$\begin{array}{r}
 14 \\
 - 5 \\
 \hline
 \Rightarrow 14 + (2^1\text{'s complement of } 5)
 \end{array}$$


(2¹'s complement of (6101)S → 1011)

$$\begin{array}{r}
 1110 \rightarrow 14 \\
 + 1011 \rightarrow 2^1\text{'s complement of } 5 \\
 \hline
 \end{array}$$

$$(1) 1001 \rightarrow 9.$$

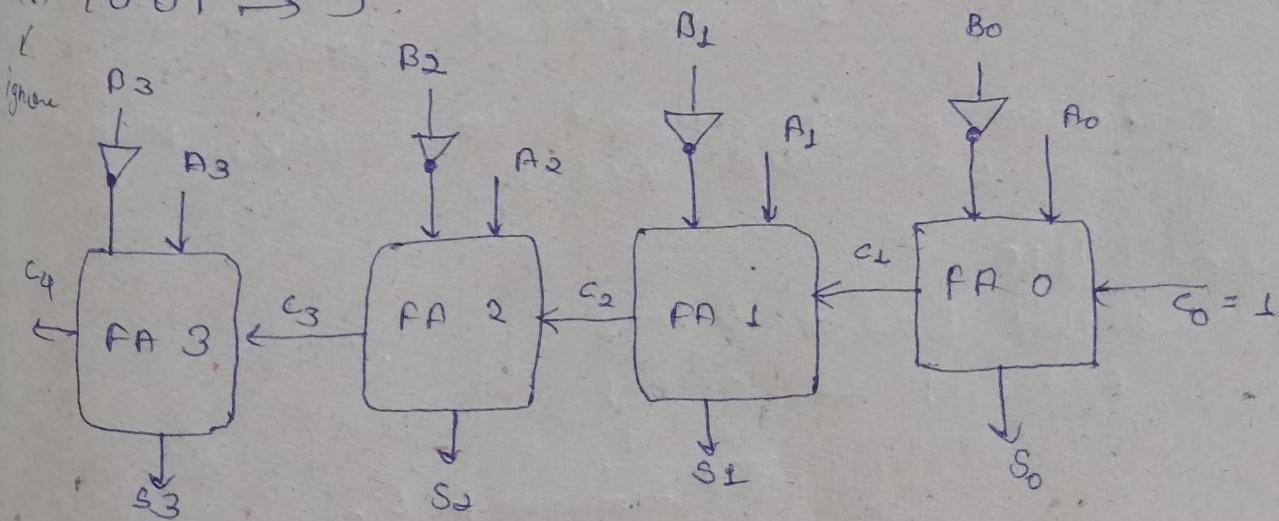

• 4 bit Adder/Subtractor -

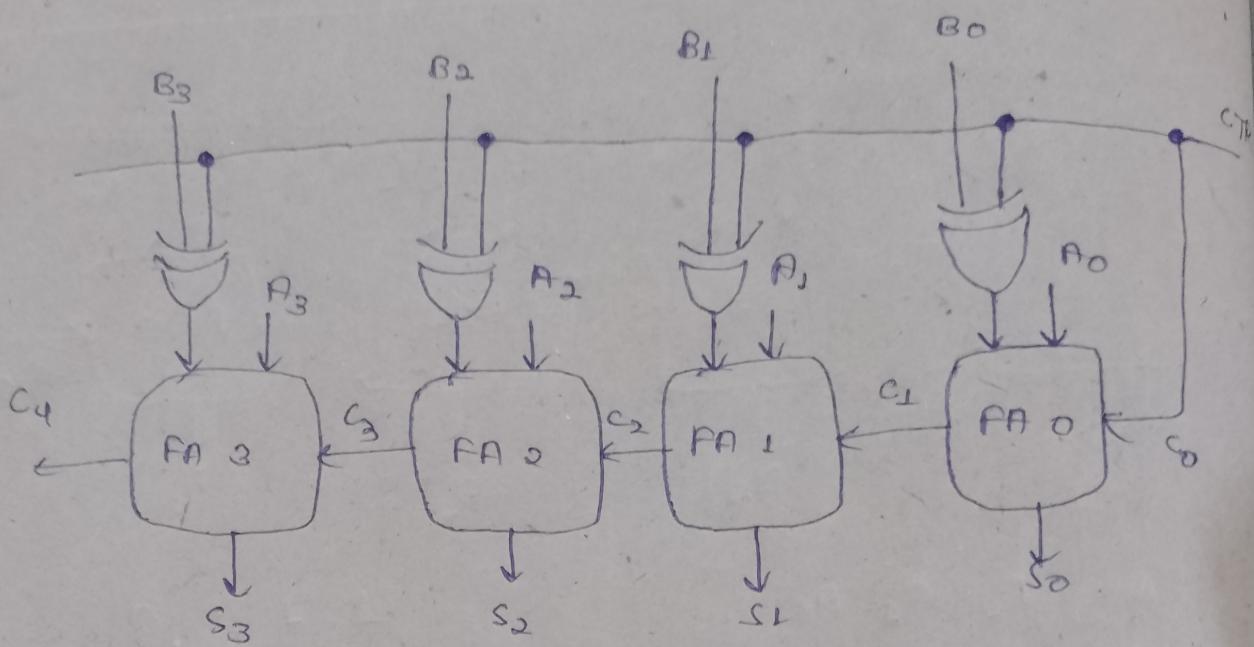

This circuit can be used for both addition and subtraction.

CTR will be 1 in case of subtraction
and 0 in case of addition.

10 (A) when $A < B$ and the answer has no
-12 (B) carry then the answer is in
+ve's complement form:



$$10 \text{ } 10 \rightarrow 10$$

$$\underline{01 \text{ } 00} \rightarrow \text{2's complement of } 12$$

$$\underline{11 \text{ } 10} \rightarrow \text{2's complement form}$$

To convert 2's complement to binary, invert all the bits and add 1.

$$\text{Ex- } 1110$$

short bits - 0001

$$\text{Add } 1 \rightarrow \begin{array}{r} 0001 \\ + 1 \\ \hline 0010 \end{array}$$

$$\begin{array}{r} 0010 \\ + 1 \\ \hline 0011 \end{array} \rightarrow \text{Ans}$$